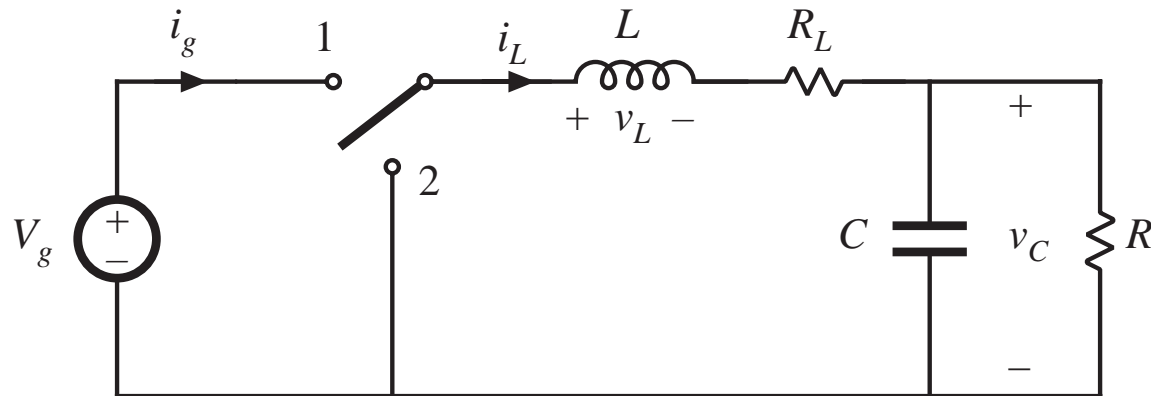


### 3.4. How to obtain the input port of the model

Buck converter example — use procedure of previous section to derive equivalent circuit




Average inductor voltage and capacitor current:

$$\langle v_L \rangle = 0 = DV_g - I_L R_L - V_C \qquad \langle i_C \rangle = 0 = I_L - V_C/R$$
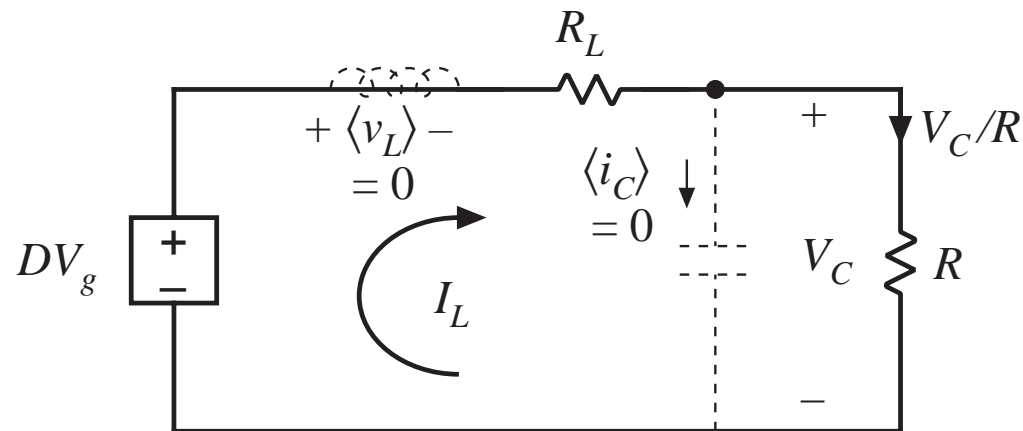
## Construct equivalent circuit as usual

$$\langle v_L \rangle = 0 = DV_g - I_L R_L - V_C$$

$$\langle i_C \rangle = 0 = I_L - V_C/R$$




What happened to the transformer?

- Need another equation

# Modeling the converter input port

Input current waveform  $i_g(t)$ :

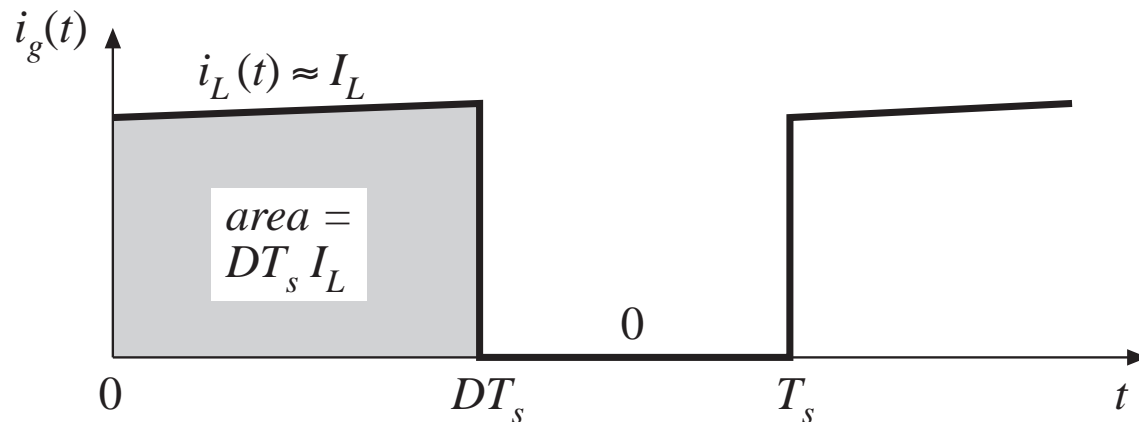


Dc component (average value) of  $i_g(t)$  is

$$I_g = \frac{1}{T_s} \int_0^{T_s} i_g(t) dt = DI_L$$
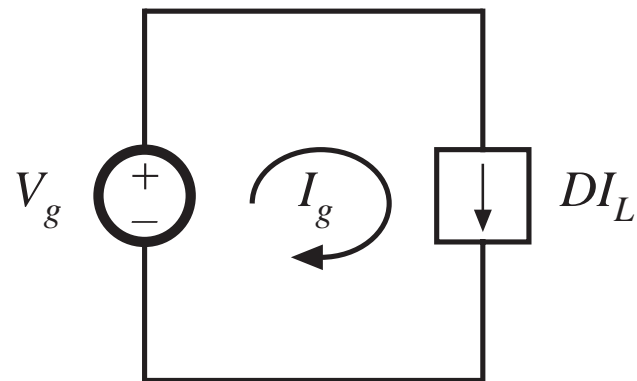
# Input port equivalent circuit


---

$$I_g = \frac{1}{T_s} \int_0^{T_s} i_g(t) dt = DI_L$$


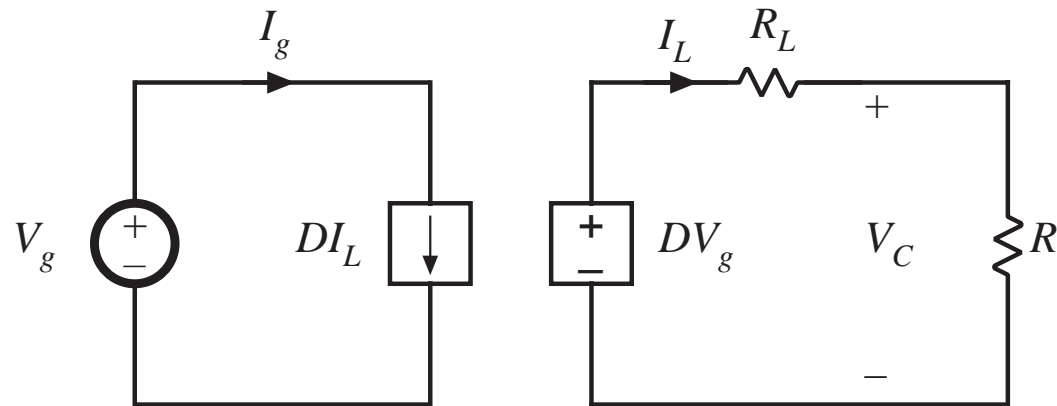
# Complete equivalent circuit, buck converter

Input and output port equivalent circuits, drawn together:



Replace dependent sources with equivalent dc transformer:

